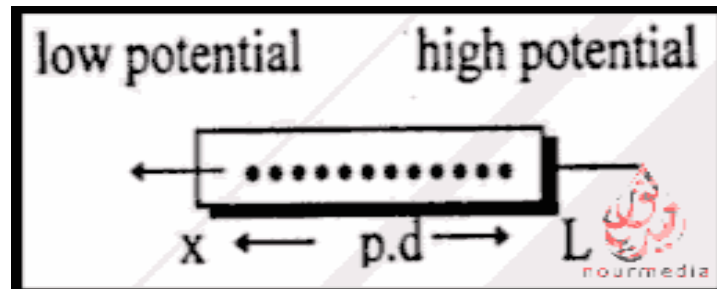


The electric current

منتدى روضة العلوم الطبيعية للثانوية

INTRODUCTION :



(1) Electric current:

“It is the flow of electric charges moving under p.d”.

The potential difference between two points on a conductor forms an electric field, which forces the electrons in the conductor.

When the electrons move they generate from electric current

(2) The electric current intensity “I” $\therefore I = \frac{Q}{t}$

It is the quantity of electricity passing through the C.S. area of a conductor per 1 second”.

(3) Unit of I “The ampere”:

$$Q = I \times t$$



“It is the intensity of elect. current if the passed quantity of elect. = 1

coulomb per one second”.

$$\therefore 1 \text{ ampere} = \frac{1 \text{ coulomb}}{1 \text{ second}}$$

(4) Types of elect, current:

o direct current (d.c) sources: batteries - cells o alternating current (a.c)

sources: dynamo

(5) Direction of current:

1- the traditional direction:-

Is the direction of motion of the (+ve) charge from high potential to low potential or from + ve pole to - ve pole (It can be noted in solutions).

2- Real direction:-

Is the direction of motion of- ve charge from - ve pole to + ve pole or from low potential to high potential.

(It can be noted in motion of electrons in a conductor).

(6) No. of electrons:

$$N_e = \frac{Q_{\text{total}}}{Q_e} \quad \text{Where } Q_e = 1.6 \times 10^{-19} \text{ coulomb}$$

(7) I of hydrogen atom :

$$I = \frac{Q_{\text{total}}}{t_{\text{total}}} = Q_e \times \text{No. of revolutions} / t$$

(8) Potential difference between two points of a conductor : -


$$\begin{array}{ccccccc} W & = & V & \times & Q & & V = \frac{W}{Q} \\ \text{(v) (p.d):} & \text{J} & & \text{volt} & \text{coulomb} & & \end{array}$$

“ It is the work done to transfer a quantity of charge 1 coulomb between the two points ”.

(9) Unit of p.d “the volt”:

It is the p.d between two points if the work done = joule to transfer a quantity of charge = 1 coulomb between the points”.

10 J required to transfer 5c? J required to transfer 1 C

$$\begin{aligned} V &= \frac{10 \text{ J}}{5 \text{ C}} = 2 \text{ J / C} \\ &= 2 \text{ volts} \\ \therefore 1 \text{ volt} &= 1 \text{ joule/coulomb} = \frac{\text{Joule}}{\text{ampere.Sec}} \end{aligned}$$


(10) Electric energy “E” :

$$\begin{array}{ccccccc} E & = & V & \times & I & \times & t \\ \text{J} & & \text{volt} & & \text{ampere} & & \text{s} \end{array}$$

“It is the work done in any interval of time”

(11) Ohm’s law:

$$\begin{array}{ccccccc} V & = & I & \times & R \\ \text{volt} & & \text{ampere} & & \text{ohm} \end{array}$$

(12) Electric power “P” :

“ It is the work done per second ”

$$\backslash P = \frac{E}{t} = \frac{VIt}{t}$$

$$Watt = J/S$$

$$\backslash P = IV = I^2 R = \frac{V^2}{R}$$

$$1 \text{ watt} = J/S = \text{Amp. volt} = \text{Amp}^2 \cdot \text{ohm} = \text{volt}^2 / \text{ohm}$$

(13) what is meant by :

A written expression on a lamp (220 V - 40 W)? This means that lamp works well at 220 V and consumes electric energy of 40 joule/S.

A work of 220 J required to transfer unit charge between the terminals of the lamp.

(14) The electric cell:

“ It is a source for d.c & electric energy, in which chemical energy electric energy ”



(15) The electro motive force of a cell (E.M.F):

“It is the total work done to transfer 1 coulomb In all parts of the electric circuit (Outside & inside the cell)”.

$$E = W \text{ total} = W \text{ ext.} + W \text{ int.}$$

$$= V \text{ ext.} + V \text{ int.} = IR + Ir = I(R+r)$$



$$I = \frac{E}{R + r}$$

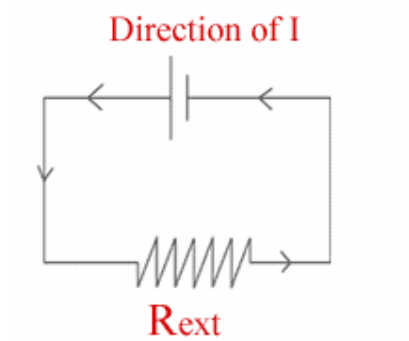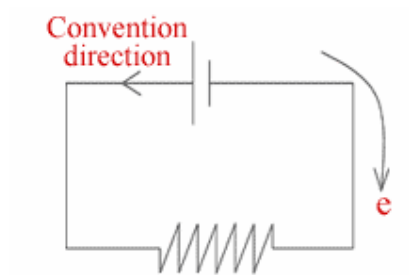

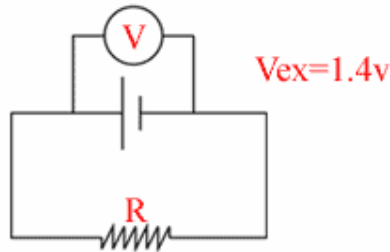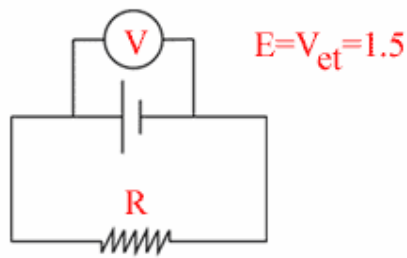(16) when the E.m.f equals the external voltage only ?

If the internal voltage = 0

$E = V_{\text{ext}} + V_{\text{int}} = 0$ "r" neglected
open circuit



Note : another definition of E.m.f:

“It is the external p.d between the two terminals of the cell in case of opened circuit” (no current passes through it).

When the external resistance increase, I decrease The internal voltage:

When the external resistance increases, the terminal voltage increases.

When the external resistance increases, the internal voltage decreases.

But we have no direct prop. between R and V_R because the prop.

Constant is absent .