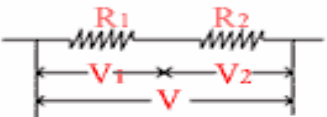
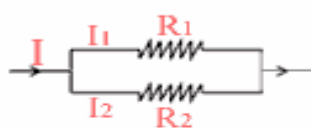


Series and parallel connection of a group of resistors

منتدى روضة العلوم الطبيعية

Grouping of resistors

I- In series	II- In parallel
 <p>(1) I constant</p> <p>(2) V divides: $\frac{V_1}{V_2} = \frac{R_1}{R_2}$</p>	 <p>V constant</p> <p>I divides: $\frac{I_1}{I_2} = \frac{R_1}{R_2}$</p>
<p>(3) Total R (R_{eq})</p> <p>The prove: -</p> <p>$V_T = V_1 + V_2 + \dots$</p>	<p>$I_T = I_1 + I_2 + \dots$</p> <p>$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$</p>

NOTCS:-

1- in case of two resistors in parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \longrightarrow \therefore \frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 \times R_2}$$

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} \longrightarrow \frac{\text{product}}{\text{sum}}$$

2- Distribution of in two branches in parallel





$$\therefore V_1 = V_2$$

$$\therefore I_1 R_1 = I_2 R_2$$


$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$\therefore \left(\frac{I_1}{I_1 + I_2} \right) = \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\therefore I_1 = I_{\text{total}} \frac{R_2}{R_1 + R_2}$$
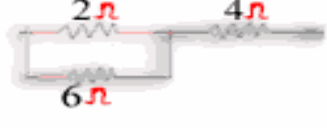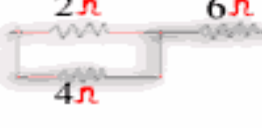
<p>(3) Examples: find the R_{eq}</p> <p>$R_{eq} = 2+4+6 = 12$</p> 	<p>of the following groups:</p> $\frac{1}{R} = \frac{1}{2} + \frac{1}{4} + \frac{1}{6} = \frac{6+3+2}{12} = \frac{11}{12}$ $\therefore R_{eq} = \frac{12}{11} \Omega$ 
$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{6} = \frac{4}{6} \quad \therefore R = 1 \frac{1}{2}$ $\therefore R_{eq} = 4 + 1 \frac{1}{2} = 5 \frac{1}{2} \Omega$ 	$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \quad \therefore R = 1 \frac{1}{3}$ $\therefore R_{eq} = 1 \frac{1}{3} + 6 = 7 \frac{1}{3} \Omega$  <p style="text-align: right;">nourmedia</p>

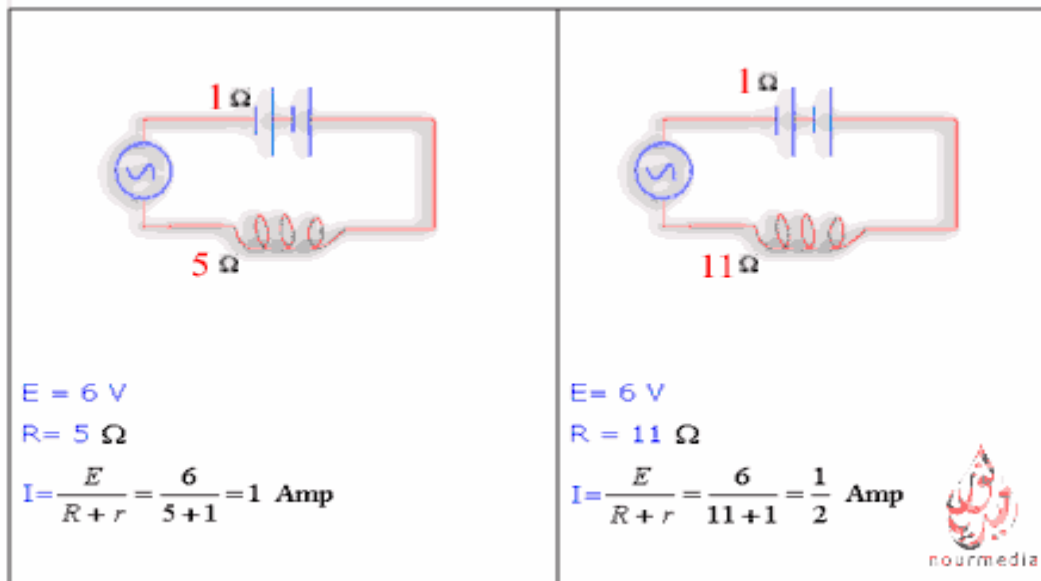The relation between external resistance and terminal voltage



When the resistance increases, the current decreases.


$V_R = IR$ $1 \times 5 = 5 \text{ volt}$	$V = IR$ $V = \frac{1}{2} \times 11 = 5.5 \text{ VOLT}$
---	--

When the resistance increases the terminal voltage increases but there is no direct prop. Between them because there is no prop .Constant.


$V_r = IR$ $= 1 \times 1 = 1 \text{ volt}$	$V = IR$ $V = \frac{1}{2} \times 1 = 0.5 \text{ volt}$
---	---

*Internal voltage decreases when R increases


FIND I_b

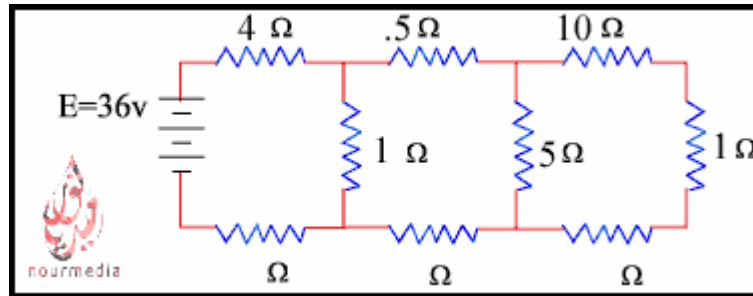
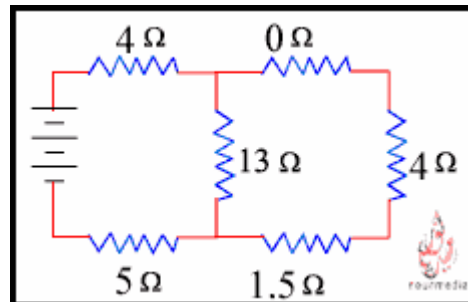
$$R_{eq} = \frac{20 \times 5}{25} = 4\Omega$$


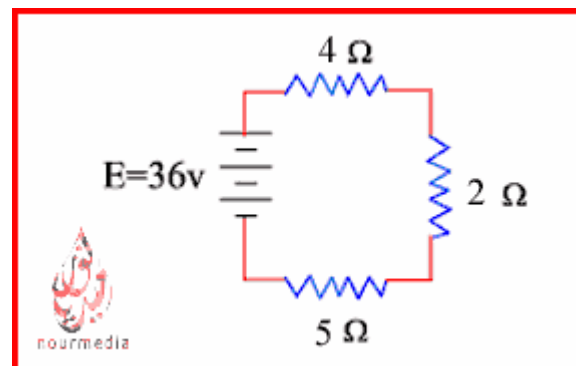
$$R_{eq} = \frac{6 \times 3}{9} = 2\Omega$$



$$R_{total} = 11\Omega$$

$$I_b = \frac{E}{R + r} = \frac{36}{11 + 1} = 3Amp$$

منتدي روضة العلوم الطبيعية